


Current Electricity

- A current i is passing through a wire having two sections P and Q of uniform diameters d and $d/2$ respectively. If the mean drift velocity of electrons in sections P and Q is denoted by v_P and v_Q respectively, then
 - $v_P - v_Q$
 - $v_P = \frac{1}{2} v_Q$
 - $v_P = \frac{1}{4} v_Q$
 - $v_P = 2v_Q$
- An ionization chamber with parallel conducting plates as anode and cathode has 5×10^7 electrons and the same number of singly-charged positive ions per cm^3 . The electrons are moving at 0.4 m/s . The current density from anode to cathode is $4 \mu A/m^2$. The velocity of positive ions moving towards cathode is
 - 0.4 m/s
 - 1.6 m/s
 - Zero
 - 0.1 m/s
- A rod of a certain metal is 1.0 m long and 0.6 cm in diameter. Its resistance is $3 \times 10^{-3} \Omega$. Another disc made of same metal is 2.0 cm in diameter and 1.00 mm in thick. What is the resistance between the round faces of the disc
 - $1.35 \times 10^{-8} \Omega$
 - $2.7 \times 10^{-7} \Omega$
 - $4.05 \times 10^{-6} \Omega$
 - $8.1 \times 10^{-5} \Omega$
- Two wires of brass of diameter 1 mm and 2 mm have equal weight. Their electrical resistance will be in the ratio
 - $16 : 1$
 - $1 : 16$
 - $1 : 4$
 - $4 : 1$
- The resistance of the series combination of two resistances is S . When they are joined in parallel the total resistance is P . If $S = n P$ then the Minimum possible value of n is
 - 2
 - 3
 - 4
 - 1
- Two resistances R_1 and R_2 are made of different materials. The temperature coefficient of the material of R_1 is α and of the materials of R_2 is $-\beta$. The resistance of the series combination of R_1 and R_2 will not change with temperature, if R_1/R_2 equals
 - $\frac{\alpha}{\beta}$
 - $\frac{\alpha + \beta}{\alpha - \beta}$
 - $\frac{\alpha^2 + \beta^2}{\alpha\beta}$
 - $\frac{\beta}{\alpha}$
- When connected across the terminals of a cell, a voltmeter measures 5 V and a connected ammeter measures 10 A of current. A resistance of 2 ohms is connected across the terminals of the cell. The current flowing through this resistance will be
 - 2.5 A
 - 2.0 A
 - 5.0 A
 - 7.5 A
- A battery is first connected in parallel to resistor R_1 and then R_2 . The value of R_0 of internal resistance of battery for which heat released in external circuit be same in both cases is
 - $\frac{R_1 R_2}{R_1 + R_2}$
 - $\sqrt{R_1 R_2}$
 - $R_1 R_2$
 - $\frac{R_1 R_2}{2}$
- A galvanometer of resistance 20Ω gives a full scale deflection when a current of 0.04 A is passed through it. It is desired to convert it into an ammeter reading 20 A in full scale. The only shunt available is 0.05Ω resistance. The resistance that must be connected in series with the coil of the galvanometer is
 - 4.95Ω
 - 5.94Ω
 - 9.45Ω
 - 12.62Ω
- The length of a potentiometer wire is l . A cell of emf E is balanced at a length $\frac{l}{3}$ from the positive end of the wire. If the length of the wire is increased by $\frac{l}{2}$. At what distance will the same coil give a balance point
 - $\frac{2l}{3}$
 - $\frac{l}{2}$
 - $\frac{l}{6}$
 - $\frac{4l}{3}$
- A galvanometer of resistance 36Ω is changed into an ammeter by using a shunt of 4Ω . The fraction i_0 of total current passing through the galvanometer is
 - $\frac{1}{40}$
 - $\frac{1}{4}$
 - $\frac{1}{140}$
 - $\frac{1}{10}$
- Two resistances of 400Ω and 800Ω are connected in series with 6 volt battery of negligible internal resistance. A voltmeter of resistance $10,000 \Omega$ is used to measure the potential difference across 400Ω . The error in the measurement of potential difference in volts approximately is
 - 0.01
 - 0.02
 - 0.03
 - 0.05

GRAVITY CLASSES


13. In the following circuit current i_1 is

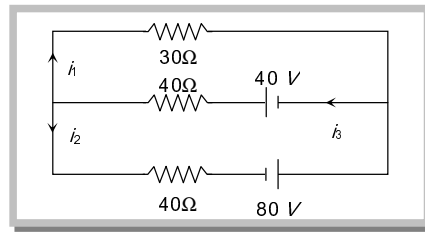- (a) 0.4 A
- (b) -0.4 A
- (c) 0.8 A
- (d) -0.8 A



14. The reading of ammeter in the adjoining diagram will

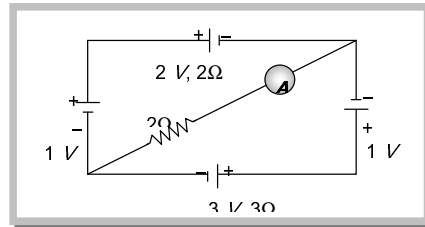- (a) $\frac{2}{17} A$
- (b) $\frac{3}{11} A$
- (c) $\frac{1}{13} A$
- (d) $\frac{4}{15} A$



15. In the following part of a circuit, what will be the potential difference between A and B i.e. ($V_B - V_A$)

- (a) 3 V
- (b) 15 V
- (c) -5.1 V
- (d) +5.1 V

